

Lesson 12

Testbench (Combinational Logic)

Mohd Saufy Rohmad

Technical Trainer and Consultant

Testbench

- A major part of digital design is testing with simulation.
- A designer should never be satisfied if a VHDL code doesn't show any compilation or synthesis error.
- The design needs to be simulated with different inputs to see whether we are getting the correct output.
- The question is, how to simulate a circuit written in VHDL?
- There comes the testbenches.
- A testbench is another entity that takes the design under test (DUT) as a component.
- In this lesson, we will talk about testbenches written for combinational logics.
- We wrote an 8-bit adder in lesson 5. The entity was written as:

```
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;  
entity adder_8bitc is  
port (  
    A,B: in unsigned(7 downto 0);  
    C : out unsigned(8 downto 0) );  
end adder_8bitc;
```

```
architecture adder_8bitc_arch of adder_8bitc is  
begin  
    C <= resize(A+B,9);  
end adder_8bitc_arch;
```

Testbench

- We want to test this circuit.
- So we need a testbench.
- We create an entity testbench_tb that doesn't have any input or output ports.
- This entity contains the adder_8bitc entity as a component.
- The input and output ports are connected to a few signals instantiated in the testbench_tb entity.
- We can feed these signals with different input values at different time instances and check the output.
- The code of the testbench is given below,

```
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;
```

```
entity testbench_tb is  
end testbench_tb;  
architecture testbench_arch of testbench_tb is  
component adder_8bitc is  
port (  
A,B: in unsigned(7 downto 0);  
C : out unsigned(8 downto 0) );  
end component;  
signal A: unsigned(7 downto 0) := (others=>'0');  
signal B: unsigned(7 downto 0) := (others=>'0');  
signal C: unsigned(8 downto 0) := (others=>'0');
```

```
begin
adder_8bi: adder_8bitc port map(
```

```
A => A,
B => B,
C => C);
```

```
process
```

```
begin
```

```
wait for 100 ns;
```

```
A <= "00000010";
```

```
B <= "00000011";
```

```
wait for 10 ns;
```

```
A <= "00000110";
```

```
B <= "00000101";
```

```
wait;
```

```
end process;
```


```
end testbench_arch;
```

Testbench

- In this case, we fed the inputs of `adder_8bi` with some values after 100ns.
- Then we wait for 10ns and feed next input values again.
- Afterwards, we wait indefinitely.
- Recall lesson 10, where we stated how behavioral codes use some extra features of VHDL language that are not supported for synthesis.
- The wait statements are not synthesizable.
- However, we don't also want to synthesize the testbench.
- We just want to use this part of the code for testing.

Run on ModelSim

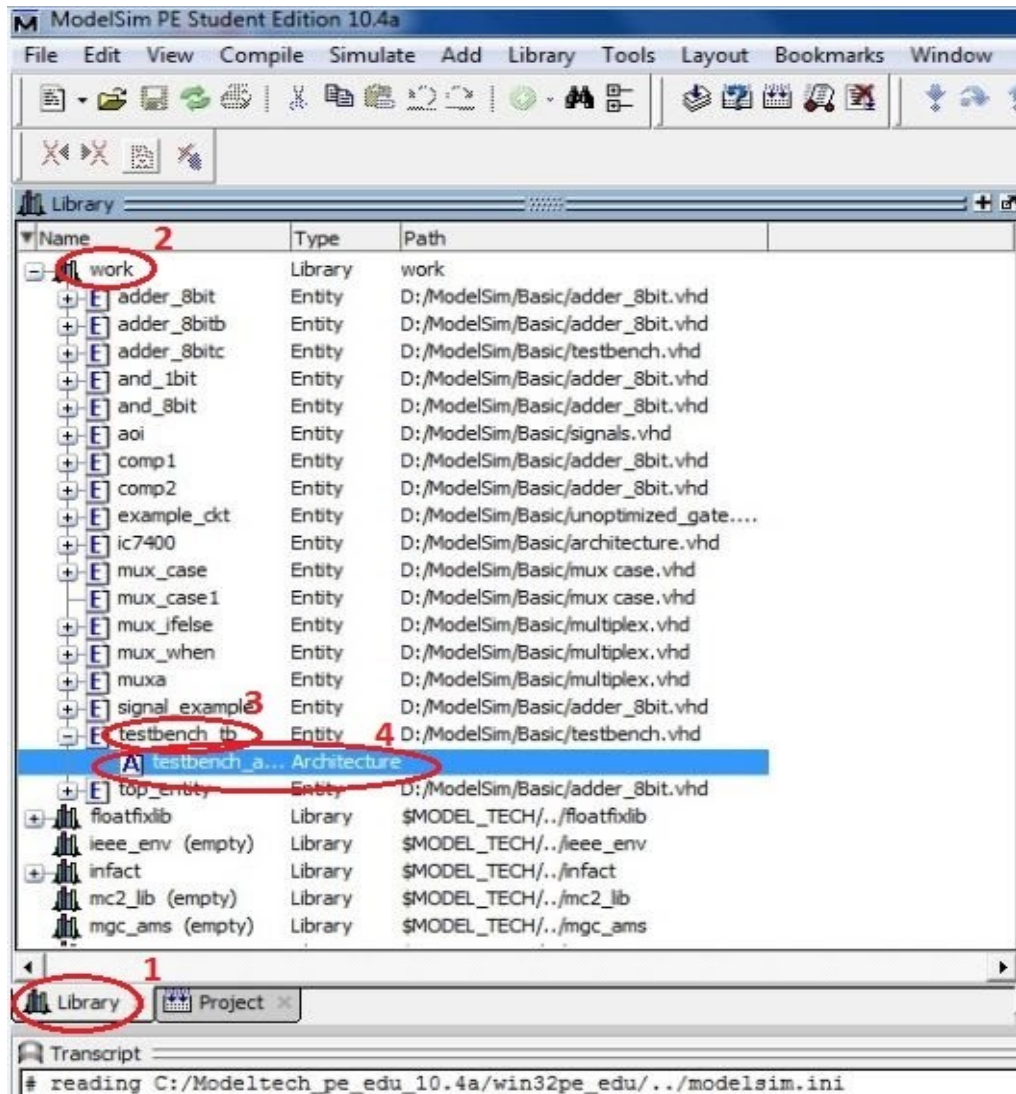- After compiling the above code click on the "library" (circle 1)>click on "work" (circle 2)>click "testbench_tb" (circle 3) as the project name was that. Then you will find the architecture file. Right click on that and select "Simulate".



ModelSim PE Student Edition 10.4a

File Edit View Compile Simulate Add Source Tools Layout Bookmarks Window Help

500 ns

Layout Simulate

ColumnLayout AllColumns

sim - Default

Instance	Design unit	Design unit type	Top Category	Visibility	Total coverage
testbench_tb	testbench_...	Architecture	DU Instance	+acc=...	
+ adder_8bi	adder_8bit...	Architecture	DU Instance	+acc=...	
line_57	testbench_...	Process	-	+acc=...	
standard	standard	Package	Package	+acc=...	
textio	textio	Package	Package	+acc=...	
std_logic_1164	std_logic_1...	Package	Package	+acc=...	
numeric_std	numeric_std	Package	Package	+acc=...	

D:/ModelSim/Basic/testbench.vhd (/testbench_tb) - Default

Ln#	
49	
50	adder_8bi: adder_8bitc port map(
51	A => A,
52	B => B,
53	C => C);
54	
55	
56	process
57	begin
58	
59	wait for 100 ns;
60	
61	
62	A <= "00000010";
63	B <= "00000011";
64	
65	wait for 10 ns;
66	
67	A <= "00000110";
68	B <= "00000101";
69	
70	wait;
71	
72	
73	end process;
74	
75	
76	
77	end testbench_arch;



Library Project sim

Transcript

```
# Loading ieee.numeric_std(body)
# Loading work.testbench_tb(testbench_arch)
# Loading work.adder_8bitc(adder_8bitc_arch)

VSIM 9>
```

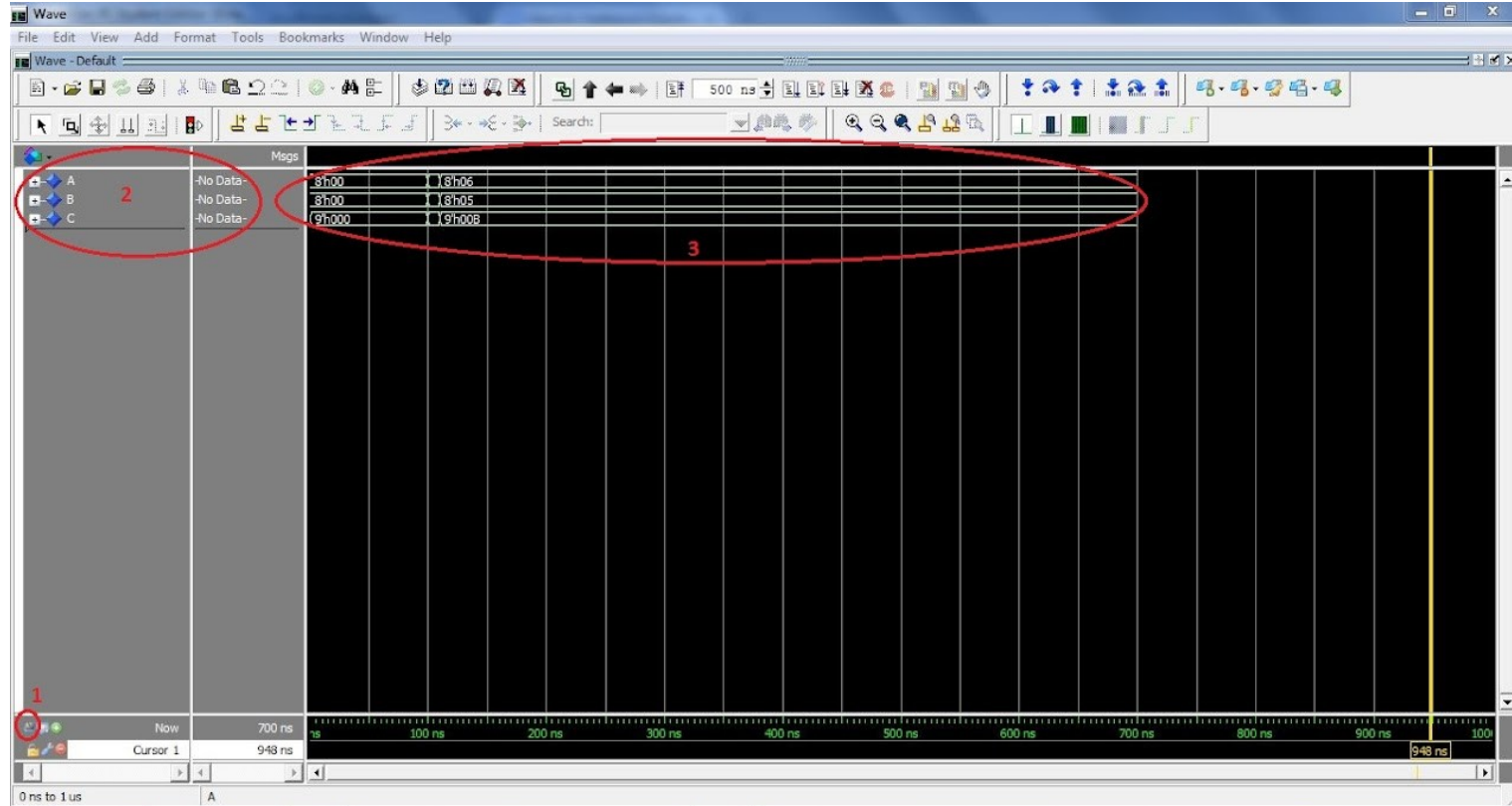 Ln: 62 Col: 0 Project: testbench Now: 0 ns Delta: 0 testbench_tb



Thank You