

Lesson 10

Combinational Logic

Mohd Saufy Rohmad


Technical Trainer and Consultant

Simple Combinational Logic

- Any section of logic that doesn't have any memory elements is considered as a combinational logic.
- So the simplest combinational logic represents a wire, for example,
- `wire1 <= wire2;`
- It means wire2 is connected to wire1.
- As mentioned in the previous lesson, we can create logic gates in the following way (lesson 5),
- `Q <= AB + BC(B+C);`
- We can visualize this logic here. Note that, A, B, C and Q are all translated as ports/wires.


Simple Combinational Logic

 - We can also write simple arithmetic units in this fashion (Hour 8),
- `C <= resize(A+B,9);`
- Here, A and B both have 8 wires to support 8-bit inputs. C has 9 wires for 9-bits.



Conditional Statements

- We will encounter scenarios where we need a conditional statements.
- How can we use conditional statements as combinational logic? We will see that in this section.
- As an example, we will create the most basic 2:1 multiplexers with several conditional statements.
- Lets assume our multiplexer is selecting between inputs A and B based on the value of "Selector". If Selector is 0, the output will be A and if Selector is 1, the output will be B.

 

When / Select

- It is possible to design the multiplexer with when-select keyword. The code is given below,

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity mux_when is
port (
    A,B: in unsigned(7 downto 0);
    Selector: in std_logic;
    C : out unsigned(7 downto 0) );
end mux_when;

architecture mux_when_arch of mux_when is
begin
    C <= A when (Selector = '0') else B;
end mux_when_arch;
```

When / Select

- When-select is very useful for writing short codes. Another example of the when-select is,

C <= "1000" when selector = "00" else

"0100" when selector = "01" else

"0010" when selector = "10" else

"0001" when selector = "11";

With/Select/When

- It is possible to design the multiplexer with with-select keyword.
- It is very similar to When-Select. The code is given below,
Library ieee;

```
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;  
entity mux_with is  
port(  
  A,B: in unsigned(7 downto 0);  
  Selector: in std_logic;  
  C: out unsigned(7 downto 0));  
end mux_with;
```

```
architecture mux_with_arch of mux_with is  
begin  
  with selector select  
    C <= A when '0',  
        B when others;  
end mux_with_arch;
```

- With-select-when can also be very useful, for example,
with selector select C <=

"1000" when "00",

"0100" when "01",

"0010" when "10",

"0001" when "11";

Process (if else statement)

- We will introduce a very important construct for the VHDL language called process. Any if-else or case statement should be inside the process construct.

- Any process should have the following structure,

process(sensitivity_list)

begin

VHDL_code (if-else and case statements goes here)

end process;

A 2:1 multiplexer can also be written with if-else inside a process as,

Process (case statement)

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity mux_ifelse is
port (
  A,B: in unsigned(7 downto 0);
  Selector: in std_logic;
  C : out unsigned(7 downto 0) );
end mux_ifelse;

architecture mux_ifelse_arch of mux_ifelse is
begin
  process(A,B,Selector)
  begin
    if Selector = '0' then
      C <= A;
    else
      C <= B;
    end if;
  end process;
end mux_ifelse_arch;
```

Thank You