

## Lesson 11


# Combinational Logic (part 2)

Mohd Saufy Rohmad

Technical Trainer and Consultant

 
# if-else vs case

- In the last hour we demonstrated how to design a 2:1 multiplexer with if-else and case.
- So one might think that logic constructed with if-else and case will be same always.
- But its not.
- Whenever we are going for more than 2 inputs in a multiplexer, then if-else and case creates different type of logic.
- Take a look at the following code,


 
# if-else vs case

- To create a 4:1 mux, we need to use the following VHDL with a case statement,



```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity mux_case is
port (
    A,B,C,D: in std_logic;
    Selector: in std_logic_vector(1 downto 0);
    E : out std_logic );
end mux_case;

architecture mux_case_arch of mux_case is
begin
    process(A,B,C,D,Selector)
    begin
        case Selector is
            when "00" => E <= A;
            when "01" => E <= B;
            when "10" => E <= C;
            when others => E <= D;
        end case;
    end process;
end mux_case_arch;
```

# Latch Inference

- We have to be very careful while writing the if-else and case statements.
- If they are not written properly, a latch can be created at the output.
- This latches can mess up the whole timing result.
- Therefore, the circuit might give wrong results at the output.

# Sensitivity List

- The sensitivity list includes all the signals that works as an input in a combinational process.
- The signals of the sensitivity list are included in the parentheses next to the process keyword in VHDL.

**process(sensitivity list)**

- In the example given above, A,B,C,D and Selector are all input signals of the 4:1 multiplexer. Thats why all of them should be in the sensitivity list.

**process(A,B,C,D,Selector)**

- Include all the input signals in the process sensitivity list for combinational logic
- Failure to include all the input signals would result in a unwanted behavior in the simulation. This is one of the most common mistakes of VHDL.

# If-Else

- This if-else is wrongly written,

```
process(state)
```

```
begin
```

```
  if state = "001" then
```

```
    cs <= "01";
```

```
  elsif state = "010" then
```

```
    cs <= "10";
```

```
  elsif state = "100" then
```

```
    cs <= "11";
```

```
  end if;
```

```
end process;
```

# If / else

- Because, it did not specify each possible state. This will create output latches. The correctly written case statement would be,

```
process(state)
begin
  if state = "001" then
    cs <= "01";
  elsif state = "010" then
    cs <= "10";
  elsif state = "100" then
    cs <= "11";
  else
    cs <= "00";
  end if;
end process;
```

# Case

- This case statement is wrongly written,

```
process(state)
begin
  case(state) is
  when "001" =>
    cs(0) <= '1';
  when "010" =>
    cs(1) <= '1';
  when "100" =>
    cs(1 downto 0) <= "11";
  when others =>
    cs(1 downto 0) <= "00";
  end case;
end process;
```



# Case

- Because, it did not specify all possible outputs for each state.
- This will create output latches. The correctly written case statement would be:

```
process(state)
```

```
begin
```

```
  cs <= "00";
```

```
  case(state) is
```

```
when "001" =>
```

```
...
```

Thank You